

(1)

Subject: microwave electronics

Level: 5

Mis-Term exam. Summer 2018

1-a Model Answer

$$Z_i(z) = z_0 \frac{(z_L + j z_0 \tan \beta L)}{z_0 + j z_L \tan \beta L} \Rightarrow \begin{array}{l} \text{At S.F: } z_L = 0 \\ \text{At o.c } z_L = \infty \end{array}$$

B. L Band 1-2 GHz — X Band 8-12 GHz

$$B - \Gamma(0) = \frac{z_L - z_0}{z_L + z_0} = \frac{75 - 50}{75 + 50} = 0.2$$

$$\Gamma\left(\frac{d}{4}\right) = \sqrt[0]{e^{-2\alpha L}} = 0.2 e^{-j2 \times \frac{2\pi}{4}} = 0.2 \times (-1) = -0.2$$

Question no 2:

2-a The process of filter design


- ① filter specification
- ② Low-pass prototype design
- ③ scaling and conversion
- ④ implementations

2-c

equal-ripple, sharp cutoff At stop Band

$G_2 - C$

(8)

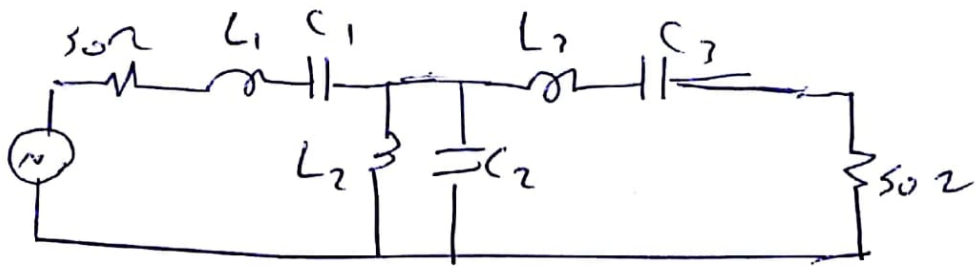

$$g_1 = 1.59$$

$$g_2 = 1.095$$

$$g_3 = 1.59$$

$$g_4 = 1$$

$$L_1' = \frac{L_1 R_0}{\omega_0 \Delta} = 127.0 \text{ nH}$$

$$C_1' = \frac{\Delta}{\omega_0 L_1 R_0} = 0.199 \text{ pF}$$

$$L_2' = \frac{\Delta R_0}{\omega_0 C_2} = 0.725 \text{ nH}$$

$$C_2' = \frac{C_2}{\omega_0 \Delta R_0} = 34.0 \text{ pF}$$

$$L_3' = \frac{L_3 R_0}{\omega_0 \Delta} = 127.0 \text{ nH}$$

$$C_3' = \frac{\Delta}{\omega_0 L_3 R_0} = 0.199 \text{ pF}$$

Q_3 :

(3)

$$\frac{w}{w_c} - 1 = \frac{4}{2.5} - 1 = 0.6$$

From the chart $N = 6$

From the table

$$g_1 = 0.517 = C_1$$

$$g_2 = 1.414 = L_2$$

$$g_3 = 1.932 = C_3$$

$$g_4 = 1.932 = L_4$$

$$g_5 = 0.517 = C_5$$

$$g_6 = 0.517 = L_6$$

Section	$Z_1 = Z_2 \text{ or } Z_n$	$BL_1 (\text{deg})$	$L_1 (\text{mm})$
1	20	11.8	2.05
2	120	0.428	5.63
3	20	11.3	7.69
4	120	0.428	9.56
5	20	11.3	5.63
6	120	0.428	2.41