

Subject: integrated circuits

No. of questions: 3

No. pages: 2

Total marks: 20marks



Subject code:

Level: 3

Time: 11:00 - 12:30 pm (1.5h)

Date: 28 /7/2018

Mid Term Examination, summer Semester 2017-2018- Dr. Amira Elsonbaty

1: What is an IC& Why are ICs more reliable than discrete circuits? ). [2 marks]

ICs are more reliable because of elimination of soldered joints and need for fewer interconnections.

2: Write short notes about IC structure & its Classification (technology, Type, Size). [1 marks]

An integrated circuit (IC) is one in which all active and passive components such as transistor, diodes; resistors, capacitors etc. are automatically part of a small semiconductor chip. ICs are more reliable because of elimination of soldered joints and need for fewer interconnections.

IC Classification

- Circuit technology (BJT, BiCMOS, NMOS, CMOS)
- Design style (Standard cell, Gate Array, Full Custom, FPGA)
- Design Type (Analog, Digital, or Mixed-Signal)
- Circuit Size (SSI, MSI, LSI, VLSI, ULSI, GSI)


3: What is the basic function of TTL gate?1 MARK

The basic function of TTL gate is NAND function. It is the most popular logic family.

4: **How many** op-amps are required to implement this equation  $V_O = V_1$ ? **Explain?** [2marks]


**One op-amp**

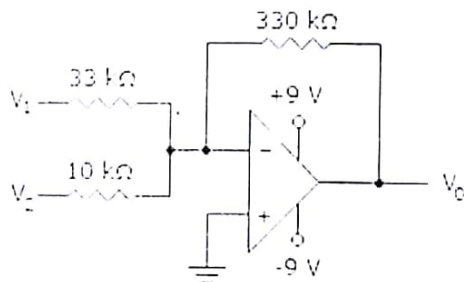5: Calculate the output voltage if  $V_1 = -0.2$  V and  $V_2 = 0$  V.[4marks ]



$$V_o = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$
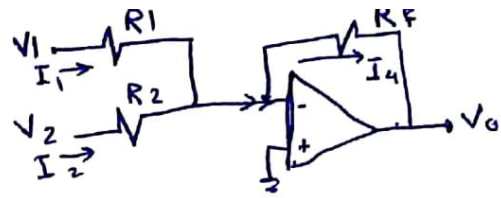
$$= -330 \left( \frac{-0.2}{33} + \frac{0}{10} \right)$$



### 3: Analysis and Design the Digital Integrated Circuit

#### Design Procedure

##### 1. Specification

- Write a specification for the circuit if one is not already available

##### 2. Formulation

- Derive a truth table or initial Boolean equations that define the required relationships between the inputs and outputs, if not in the specification

Answer: Option A

7: Transistor-transistor logic (TTL) is a class of digital circuits built from

- a) Transistors only
- b) Bipolar junction transistors (BJT)
- c) Resistors
- d) Bipolar junction transistors (BJT) and resistors

Answer: d

8: In DTL logic gating function is performed by

- a) Diode
- b) Transistor
- c) Register
- d) Capacitor

Answer: a

9: In DTL logic gating function is performed by

- a) Diode
- b) Transistor
- c) Register
- d) Capacitor

Answer: a

10. To increase fan-out of the gate in DTL

- a) An additional capacitor may be used
- b) An additional resistor may be used
- c) An additional transistor and diode may be used
- d) None of the Mentioned

Answer: c

Explanation: To increase fan-out of the gate in DTL, an additional transistor and diode may be used. Here, the fan out means the number of maximum output.

Question (2): Choose the correct answer for the following

[5 marks]

1: In a TTL circuit, if an excessive number of load gate inputs are connected, \_\_\_\_\_.

A.  $V_{OH(min)}$  drops below  $V_{OH}$

B.  $V_{OH}$  drops below  $V_{OH(min)}$

C.  $V_{OH}$  exceeds  $V_{OH(min)}$

D.  $V_{OH}$  and  $V_{OH(min)}$  are unaffected

Answer: Option B

2: The greater the propagation delay, the \_\_\_\_\_.

A. lower the maximum frequency

B. higher the maximum frequency

C. maximum frequency is unaffected

D. minimum frequency is unaffected

Answer: Option A

3: Which equation is correct?

A.  $V_{NL} = V_{IL(max)} + V_{OL(max)}$

B.  $V_{NH} = V_{OH(min)} + V_{IH(min)}$

C.  $V_{NL} = V_{OH(min)} - V_{IH(min)}$

D.  $V_{NH} = V_{OH(min)} - V_{IH(min)}$

Answer: Option D

4: ECL IC technology is faster than TTL technology.

A. True

B. False

Answer: Option A

5: CMOS is a more dominant IC technology than TTL.

A. True

B. False

Answer: Option A

6: The greater the propagation delay, the higher the maximum frequency.

A. True

B. False

Answer: Option B

6: There are four different logic level ranges for TTL and CMOS:  $V_{IL}$ ,  $V_{IH}$ ,  $V_{OL}$ , and  $V_{OH}$ .

A. True


B. False

### 3. Optimization

- Apply 2-level and multiple-level optimization
- Draw a logic diagram or provide a netlist for the resulting circuit using ANDs, ORs, and inverters
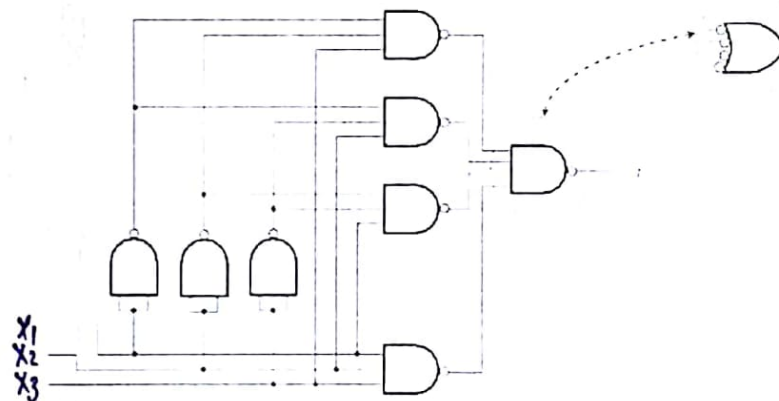
### 4. Technology Mapping

- Map the logic diagram or netlist to the implementation technology selected



### 5. Verification

- Verify the correctness of the final design

